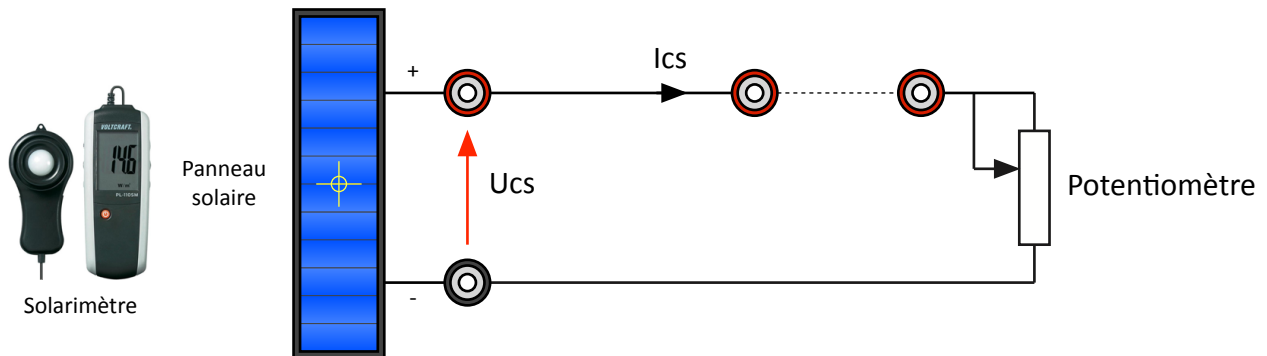


VOLET ROULANT VRS 500 – DOCUMENT RÉPONSE

Question n°1 :




Question n°3 :

I (mA)	0	4,2	4,4	4,6	...		
U (V)	...						


I (mA)							
U (V)							

I (mA)							...
U (V)							0

Question n°6 :

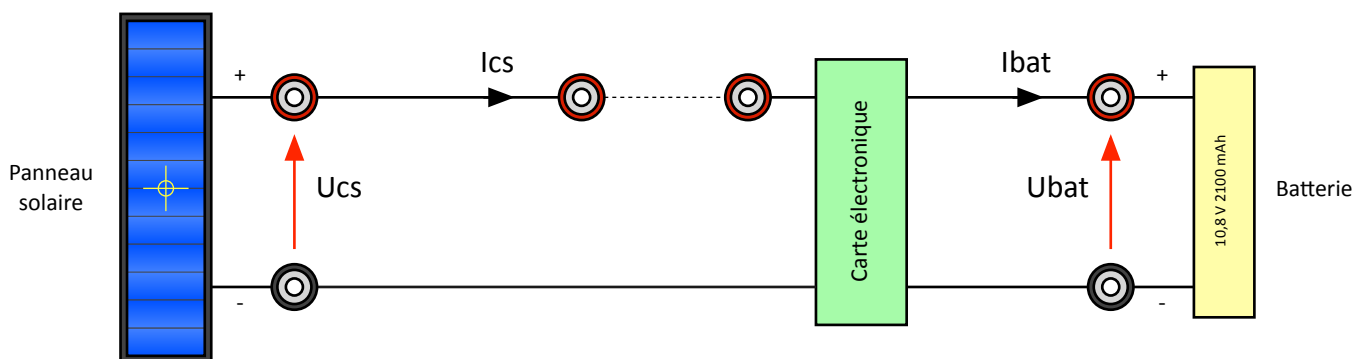

Question n°12 :

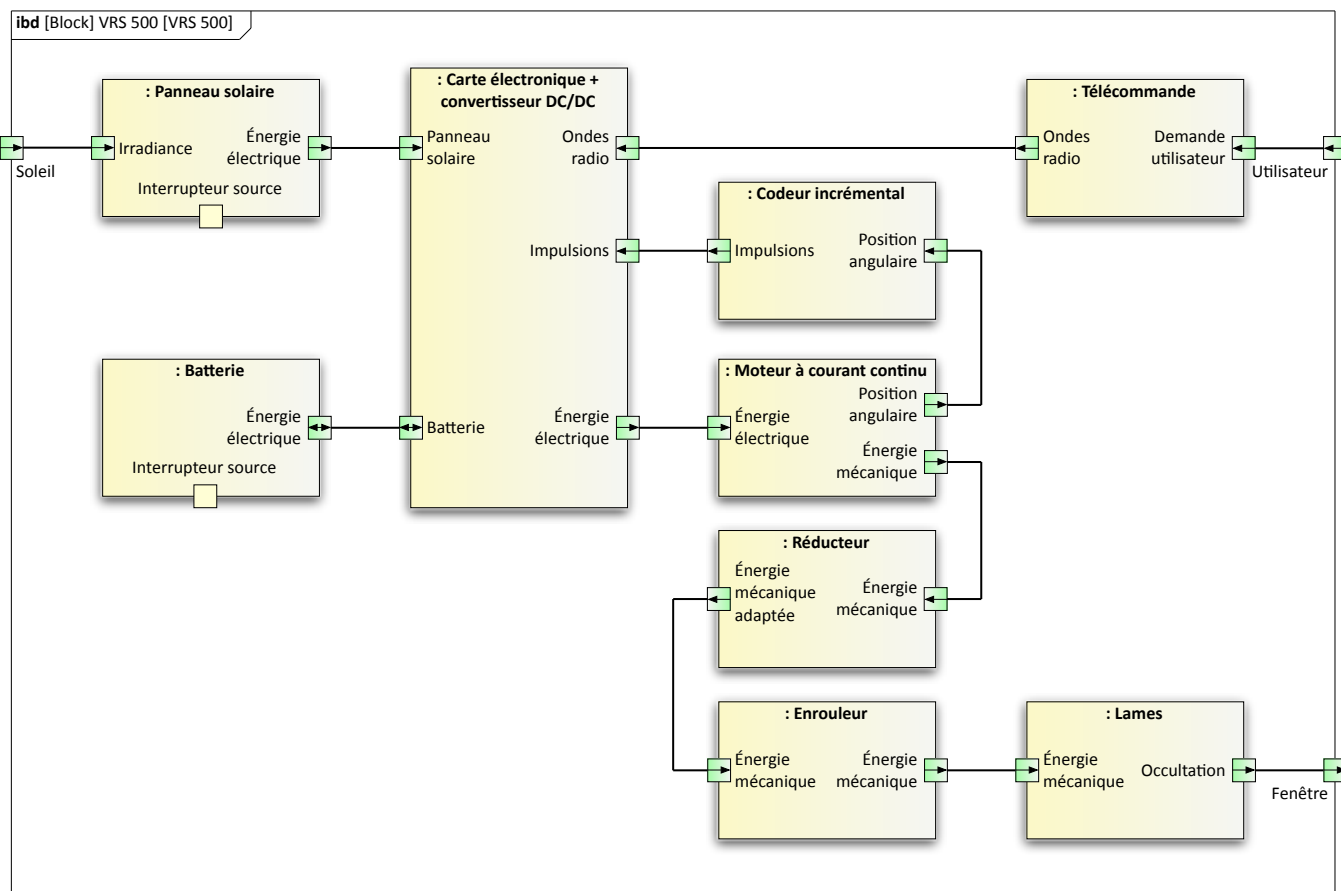

Question n°14 :

